

AUDIO Kits




NE 011 7W Mono Audio Amplifier with UL1481 (TBA810)

This small amplifier is constructed around the UL148 IC. (TBA810) The IC is fully protected against overheating and short circuits.
Music power output: 7W / 4Ohm
Frequency response: 40Hz to 20kHz
Supply voltage: 4-20V

7W 4Ω

Part No.	Ord.No
S NE 011	45263

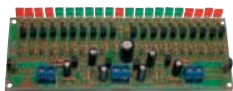

NE 012 Stereo VU Meter

It is suitable for all stereo devices as recorders, mixing consoles, stereo amplifiers...
21 LED - one for ON/OFF indication, 2x10 LED for signal - level indication
Supply voltage: 10-14V
Dimensions: 80x38x15mm

Part No.	Ord.No
S NE 012	9613



NE 013 100W Mono Audio Amplifier with TDA 7294

It is suitable for driving subwofers. The IC is fully protected against overheating and short circuits.

Music power output: 70-100W / 4Ohm
Supply voltage: from + and -10V to + and - 40V
Recommended pre-amplifier: NE025

70/100W 4Ω

Part No.	Ord.No
S NE 013	48823




NE 013 NZR 100W Mono Audio Amplifier with TDA 7294, rectifier and heatsink

This kit is suitable for driving subwofers. The IC is fully protected against overheating and short circuits.

Music power output: 70-100W / 4Ohm
Supply voltage: from + and -10V to + and - 40V
Recommended pre-amplifier: NE025

70/100W 4Ω

Part No.	Ord.No
S NE 013 NZR	62261

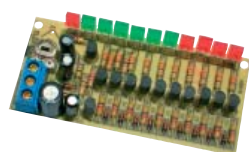

NE 016 Mono VU Meter

VU meter with a scale consisting of 10 LEDs.

Part No.	Ord.No
S NE 016	9615



NE 018 15W Mono Audio Amplifier with TDA2030

This small AF amplifier is constructed with the TDA2030 IC, with a maximum supply capability of 15Wrms/4 ohm. The IC is protected against overheating and short circuits.

Suitable for tuners, CDs, MP3, radios...


Music power output: 15W / 4Ohm

Supply voltage: max.30V

Dimensions: 55x45mm

15W 4Ω

Part No.	Ord.No
S NE 018	9617

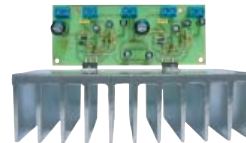

NE 019 15W Stereo Audio Amplifier with TDA2030

This small AF amplifier is constructed with the TDA2030 IC, with a maximum supply capability of 2x15Wrms/4 ohm. The IC is protected against overheating and short circuits.

Suitable for tuners, CDs, MP3, radios...

Music power output: 2x15W / 4Ohm

Supply voltage: max.30V

2x15W 4Ω

Part No.	Ord.No
S NE 019	9618



NE 020 20W Mono Audio Amplifier with TDA2003

Simple amplifier constructed with two TDA2003 in bridge connection. The IC is fully protected against overheating and short circuits.


Music power output: 20W / 4Ohm

Supply Voltage: 8-18V

Easy to install

20W 4Ω

Part No.	Ord.No
S NE 020	9619

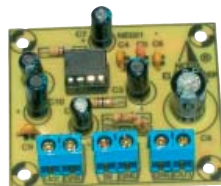

NE 021 4W Amplifier with UL1482/ TBA820M


Suitable for portable equipment

Music power output: 4W / 4Ohm

Supply Voltage: 3-16V

4W 4Ω

Part No.	Ord.No
S NE 021	45264

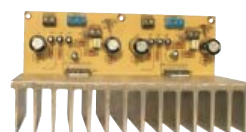

NE 022 100W Stereo Audio Amplifier with TDA7294

Suitable for driving subwofers.

Max. music power output: 2x100W / 4Ohm

Supply Voltage: from + and -10V to + and - 40V

Impedance: 4 Ohm

Recommended pre-amplifier: NE025

2x70/100W 4Ω

Part No.	Ord.No
S NE 022	48824



NE 025 Universal Low-Noise Stereo Pre-Amplifier

Suitable for NE012 (mono), NE022 (stereo) or 2xNE022

Frequency range: 20Hz - 100kHz

Max. input voltage: 775mV

Adjustable gain: ±12dB.

Input impedance: 220Kohm

Part No.	Ord.No
S NE 025	48825